

32-Bit Pipelined MIPS Processor

Matthew Bernardino
School of Engineering and Computer
Science
University of the Pacific
Stockton, USA
m_bernardino2@u.pacific.edu

Minh Dinh
School of Engineering and Computer
Science
University of the Pacific
Stockton, USA
m_dinh3@u.pacific.edu

Shaan Lele
School of Engineering and Computer
Science
University of the Pacific
Stockton, USA
s_lele@u.pacific.edu

Abstract—This report covers the design and implementation of a 32 bit pipelined MIPS processor using SystemVerilog. The processor is split into the usual stages like instruction fetch, decode, execute, memory, and write back. Each part was built and tested on its own before putting everything together. The main focus was making sure data moves correctly between stages and that instructions run the way they are supposed to. Simulation was used to test different cases and check that the processor behaves correctly. In the end, the design works as expected and shows a full working example of a pipelined processor.

Keywords—*Pipelining, SystemVerilog, RISC Architecture, Hazard Handling, Forwarding Unit, HDL Simulation, 32-bit MIPS*

I. INTRODUCTION

Modern processors rely on pipelining to improve performance by allowing multiple instructions to be processed at the same time. Instead of completing one instruction before starting the next, a pipelined design breaks instruction execution into stages, which increases overall throughput. This concept is widely used in real-world CPU design and is an important topic in computer engineering. This project focuses on the design and implementation of a 32-bit pipelined MIPS processor using SystemVerilog. The processor is divided into the standard five stages, which are instruction fetch, instruction decode, execute, memory, and write back. Each stage is connected through pipeline registers, allowing instructions to move through the system in a structured and efficient way. The goal of this work is to build each module from scratch and verify that they function correctly both individually and when integrated together. Special attention is given to how data moves between stages and how control signals are handled. Basic pipeline concepts such as instruction flow and stage separation are demonstrated through simulation and testing. This paper will go through the design of the processor, explain the purpose of each module, and show how the full system operates as a complete pipeline. The results from simulation will also be discussed to confirm that the processor behaves as expected.

II. PROCESSOR ARCHITECTURE (METHODOLOGY)

A. Control Unit

The control unit reads the 6-bit operation code field. Creates the control signals for the pipeline based on the instruction. The control signals tell the pipeline what path the data will take through the hardware like register file and ALU. The ALU uses this information to correctly do the math operation from the control signal.

B. ALU

The ALU is the arithmetic logic unit that takes two 32-bit inputs and does the math operation given to the unit from the ALU control unit. When completed, the result is saved into the execute/memory pipeline register, passed back to write back in the register file, or there is a zero flag check for operations like BEQ on whether a branch is taken or not.

III. COMPONENT IMPLEMENTATION

This processor is designed with a modular approach, so each file performs a specific task in the processor pipeline. These modules are then connected with a top-level module, ensuring data moves correctly throughout the pipeline. Since the system is organized into separate modules, it makes it easier to verify the logic paths and handle complex hazards. The following sub-sections explain every module.

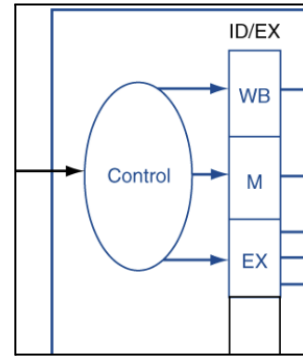


Fig. 4: Control Unit

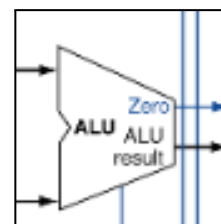


Fig. 5: ALU - Arithmetic Logic Unit

A. Top-Level Integration (Pipeline Processor 32-Bit)

The top-level module manages and connects the entire system together. It instantiates and connects all of the following submodules. Most importantly, it uses the control signals to either stall or flush the pipeline and integrates multiplexers to handle data forwarding to maintain system stability.

B. Program Counter (IF Stage)

The program counter keeps track of the current instruction address in the processor. At each clock cycle, it updates to point to the next instruction to be fetched from instruction memory. Under normal operation, the value increments by 4 to move to the next instruction, which is shown in Fig. 1, where the adder adds a constant value of 4 to the current address. This ensures that instructions are fetched in sequence. However, when a branch or jump instruction is detected, the program counter can be updated through a multiplexer to select a different address. This allows the processor to change the instruction flow when needed while still maintaining normal sequential execution otherwise.

C. Program Counter + 4 (IF Stage)

The program counter plus 4 module is responsible for calculating the next sequential instruction address. Since each instruction is 32 bits, the address increases by 4 bytes for each new instruction. This module simply adds 4 to the current program counter value and sends that result forward in the pipeline. This value is used as the default next address unless a branch or jump overrides it. It ensures that the instruction flow continues correctly during normal execution.

D. Instruction Memory (IF Stage)

The instruction memory stores all of the instructions that the processor will execute. It takes in the address from the program counter and outputs the corresponding 32-bit instruction. This module acts as a read-only memory during simulation, where the instructions are preloaded at the start. The processor depends on this module to supply the correct instruction at each clock cycle. Without it, the pipeline would not have any operations to perform.

E. Instruction Fetch/Instruction Decode Register (IF Stage)

This register sits between the instruction fetch and instruction decode stages. It stores the instruction and the program counter value so they can be used in the next stage. This allows the fetch stage to move on to the next instruction while the decode stage works on the current one. By separating these stages, the pipeline can operate more efficiently. In cases where a stall or flush is needed, this register can hold or clear its values to prevent incorrect instructions from moving forward.

F. Control Unit (ID Stage)

The control unit is in charge of looking at the 32-bit instruction and determining what operation code is decoded and then create the signal path to where it needs to go within the pipeline. The register type instructions all have the same six digit zero opcode; however, there is a function field that specifies the operation that needs to be done with the values.

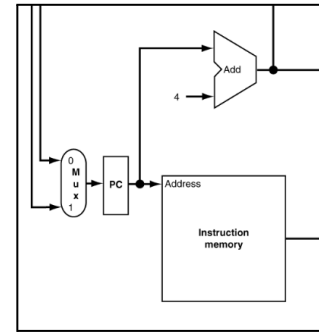


Fig. 1: Control Unit

When a R-type is known, the control signal knows that the register destination needs to be updated with the output value and what values need to be read from the registers. When it comes to the immediate type there is a different destination it is rt. When an I-type is read, there is a check for the immediate 16-bit field that needs to go to an immediate extender that will extend the 16-bit value to a usable 32-bit value. The ALU needs this to be 32 bits and so it gets extended, there is sign extension to where if the value is negative it will correctly extend the negative number; although, when using an ORI instruction, to keep the value the same it only does a zero extend as sign extending the value will cause it to be a different value.

G. Register File (ID Stage)

Within the register file we take in the instruction and analyze which registers will be used to fetch the values within them. From the control unit the signal comes in and we can determine which registers are going to be used and which need to be fetched and values. When an R-type (register) instruction is used, there is a destination register that will take the final value from the operation done between two registers. With this we need to use the write data and write register to update the register with the output. When an I-type (immediate) instruction is considered then there is the possibility that there is a value that needs to be signed extended. Since I-type uses a 16-bit immediate, the ALU needs a 32-bit value to do the operation so it needs to get passed from the register file to the immediate extender. When the values are completed and fetched then they can go to the next stage.

H. Immediate Handler (ID Stage)

The immediate handler is very straightforward in that when an I-type instruction is detected the 16-bit immediate/address field needs to be extended to 32-bits. This is because the ALU uses 32 bit values to do the operation needed. When it is being extended it does so with sign consideration. When a negative value is detected to be extended it will extend from the left in all "1's". The exception to this is that instructions like ORI cannot be sign extended and only receive a zero extension because doing a sign extension will change the value.

I. Instruction Decode/Execution Register (ID Stage)

This is a stage in which the register file has gotten the register values and taken care of any immediate extensions. When all the values and information is fetched, this stage is a transfer of data to the next state. Since the design is pipelining, freeing the register file from the values it has fetched will allow it to take on the next instruction and be independent and efficient. With this this stage transfers the

data to new variables that will then go into the next stage which is the ALU Control and ALU itself. This allows us to consider any hazards and forwarding that needs to be done before entering into the ALU to complete the operation. In this stage we can check for a reset or stall that makes all register values '0' to avoid any hazards. When all is normal and the next state is ready, we pass the values through from the register file to the variables in this stage to pass to the next stage.

J. ALU Control (EX Stage)

The ALU control is a very simple stage that receives the information of what operation code that needs to be done and specifies what operation the ALU needs to perform based on the operation code. For I-type instructions the operation is stated and easily determined within the operation code. While R-type is more specific since the operation code is the same for all R-type instructions. This unit checks the function and determines what math will be done so the ALU can do it quickly.

K. ALU (EX Stage)

The arithmetic logic unit is the main form of execution. This unit does the math that is passed from the ALU control unit. It has two inputs that are both 32-bit values. The ALU can do the following math operations: ADD, SUB, ADDI, ORI, OR, AND, and NOP in this project scope. NOP is "no operation" which passes '0' into the ALU to stall it so it does nothing while hazard or forwarding is being done. For BEQ instructions, a subtraction is done of the values to determine if a branch is taken. This is done by comparing the result to '0' and if it is then the branch is taken while if not '0' then the branch is not taken and the next instruction is done rather than going through the BEQ condition. In addition to this, LW and SW are a form of ADD or SUB in which the address offset will get the proper operation to find the proper register.

L. Execute/Memory Register (EX Stage)

The Execute/Memory Register sits between the execution stage and the memory stage. It holds the ALU's math results for the next stage. This ensures that "Store" commands have a stable address and stable data to work with when talking to the memory for one clock cycle. Without it, the ALU could start its next instruction and overwrite the current results before the Memory stage could store them since the ALU operations are faster compared to the memory operations.

M. Data Memory (MEM Stage)

The data memory module is the processor's RAM to store long term information. The memory handles two commands. LW (Load Word) can load data to registers and SW (Store Word) can save data into memory for later use. It is important because though registers are fast, they are also extremely small in capacity. The memory allows the processor to manage more data.

N. Memory/Writeback Register (MEM Stage)

The Memory/Writeback Register sits between the memory stage and the writeback stage. It holds the data coming out of the memory module, which prevents the processor from losing the data it just fetched from the memory while it prepares for the final writeback operation. This allows for the memory stage to start looking for the

next instruction's data while the current instruction is saved for the final stage.

O. Writeback Multiplexer (WB Stage)

The writeback multiplexer chooses between the ALU math result or the memory result when the load word command is used to save back into the register. This is important because it tells the processor the correct result to save back into the register.

P. Hazard Detection Unit (Hazard Management)

The hazard detection unit watches for "Load-Use" conflicts where even forwarding isn't fast enough to provide the data. "Load-Use" conflicts happen when an instruction needs data from a LW (Load Word) command immediately, so this module tells the processor to "freeze" or "stall" for one cycle. It is the safety net that prevents the processor from using outdated data if the data is not loaded from memory into the registers fast enough.

Q. Forwarding Unit (Hazard Management)

The forwarding unit intercepts a math answer from a later stage and passes it directly back to the ALU if it detects a data hazard. Suppose there are two back to back instructions (Instruction A and Instruction B). Data hazards can happen when the ALU calculates a math answer in Instruction A and the ALU tries to use that answer instantly in the next instruction (Instruction B). In this case, the Instruction A result has not had enough time to be saved into the register, so Instruction B might use the outdated answer. This allows the CPU to keep running at full speed without having to wait (stall) for the Register File to update.

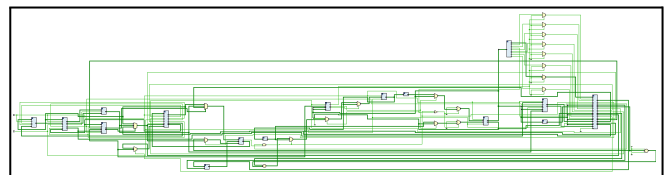


Fig. 2: 32-bit Pipelined MIPS RTL Diagram

Time=	0	PC=0		Pipeline Filling / NOP	st0x	st1x	st2x	st3x	st4x	st5x	st6x	st7x	st8x	st9x
Time=	5000	PC=0		Pipeline Filling / NOP	st0=0	st1=0	st2=0	st3=0	st4=0	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	25000	PC=4		Pipeline Filling / NOP	st0=0	st1=0	st2=0	st3=0	st4=0	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	35000	PC=8		Pipeline Filling / NOP	st0=0	st1=0	st2=0	st3=0	st4=0	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	45000	PC=12		Pipeline Filling / NOP	st0=0	st1=0	st2=0	st3=0	st4=0	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	55000	PC=16		addi st0, \$zero, 5	st0=0	st1=0	st2=0	st3=0	st4=0	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	65000	PC=20		ori st1, \$zero, 3	st0=5	st1=0	st2=0	st3=0	st4=0	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	75000	PC=24		add st2, st0, st1	st0=5	st1=3	st2=0	st3=0	st4=0	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	85000	PC=28		sub st3, st0, st1	st0=5	st1=3	st2=8	st3=0	st4=0	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	95000	PC=32		and st4, st0, st1	st0=5	st1=3	st2=8	st3=2	st4=0	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	105000	PC=36		or st5, st0, st1	st0=5	st1=3	st2=8	st3=2	st4=1	st5=0	st6=0	st7=0	st8=0	st9=0
Time=	115000	PC=40		or st5, st0, st1	st0=5	st1=3	st2=8	st3=2	st4=1	st5=7	st6=0	st7=0	st8=0	st9=0
Time=	125000	PC=44		sw st2, 0(\$zero)	st0=5	st1=3	st2=8	st3=2	st4=1	st5=7	st6=0	st7=0	st8=0	st9=0
Time=	135000	PC=48		lw st6, 0(\$zero)	st0=5	st1=3	st2=8	st3=2	st4=1	st5=7	st6=8	st7=0	st8=0	st9=0
Time=	145000	PC=52		add st7, st6, st1	st0=5	st1=3	st2=8	st3=2	st4=1	st5=7	st6=8	st7=0	st8=0	st9=0
Time=	155000	PC=56		addi st3, \$zero, -5	st0=5	st1=3	st2=8	st3=2	st4=1	st5=7	st6=8	st7=11	st8=0	st9=0
Time=	165000	PC=60		beq st2, st6, 2	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=0	st9=0
Time=	175000	PC=64		addi st0, \$zero, 99 (Skipped)	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=0	st9=0
Time=	185000	PC=68		addi st1, \$zero, 99 (Skipped)	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=0	st9=0
Time=	195000	PC=72		addi st2, \$zero, 99 (Skipped)	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=0	st9=0
Time=	205000	PC=76		add st8, st0, st1	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=0	st9=0
Time=	215000	PC=80		sub st9, st8, st0	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=8	st9=0
Time=	225000	PC=84		3 17 (Infinite Loop)	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=8	st9=3
Time=	235000	PC=88		3 17 (Infinite Loop)	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=8	st9=3
Time=	245000	PC=92		3 17 (Infinite Loop)	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=8	st9=3
Time=	255000	PC=96		3 17 (Infinite Loop)	st0=5	st1=3	st2=8	st3=5	st4=1	st5=7	st6=8	st7=11	st8=8	st9=3

Fig. 3: Functional Simulation Log

```

module instr_mem (
    input logic [31:0] addr,
    output logic [31:0] instr
);

    logic [31:0] mem [0:255];

    initial begin
        // Initialize data
        mem[0] = 32'h20080005; // addi $t0, $zero, 5 (Put 5 in $t0 - Reg 8)
        mem[1] = 32'h34090003; // ori $t1, $zero, 3 (Put 3 in $t1 - Reg 9)

        // Test math
        mem[2] = 32'h01095020; // add $t2, $t0, $t1 ($t2 (Reg 10) = 5 + 3 = 8)
        mem[3] = 32'h01095822; // sub $t3, $t0, $t1 ($t3 (Reg 11) = 5 - 3 = 2)
        mem[4] = 32'h01096024; // and $t4, $t0, $t1 ($t4 (Reg 12) = 5 AND 3 = 1)
        mem[5] = 32'h01096825; // or $t5, $t0, $t1 ($t5 (Reg 13) = 5 OR 3 = 7)

        // Test memory and stalling for "load-use" hazard
        mem[6] = 32'hAC0A0000; // sw $t2, 0($zero) (Store 8 into memory address 0)
        mem[7] = 32'h8C0E0000; // lv $t6, 0($zero) (Load from memory address 0 into $t6 - Re
        mem[8] = 32'h1C97820; // add $t7, $t6, $t1 ($t7 (Reg 15) = 8 + 3 = 11) - Testing haz

        // Test negative number
        mem[9] = 32'h200BFFFB; // addi $t3, $zero, -5 (Put -5 in $t3 - Reg 11)

        // Test branch and jump (Shifted down by 1)
        mem[10] = 32'h114E0002; // beq $t2, $t6, 2 (If $t2(8) == $t6(8), skip the next 2 in
        mem[11] = 32'h20080063; // addi $t0, $zero, 99 (Should be skipped)
        mem[12] = 32'h20090063; // addi $t1, $zero, 99 (Should be skipped)

        // Jump the next instruction
        mem[13] = 32'h0800000F; // j address 15 (Jump past the next instruction)
        mem[14] = 32'h200A0063; // addi $t2, $zero, 99 (Should be skipped)

        // Test forwarding module
        mem[15] = 32'h0109C020; // add $t8, $t0, $t1 ($t8 (Reg 24) = 5 + 3 = 8)
        mem[16] = 32'h0308C822; // sub $t9, $t8, $t0 ($t9 (Reg 25) = 8 - 5 = 3)

        // End of test
        mem[17] = 32'h08000011; // j address 17 (Loop to stop the program)

        // Initialize extra remaining memory slots to 0
        for (integer i = 18; i < 32; i++) begin
            mem[i] = 32'd0;
        end
    end

    // Word align the address (addr[31:2])
    assign instr = mem[addr[31:2]];

endmodule

```

Fig. 4: Instruction Memory (instr_mem) Initialization

IV. SIMULATION AND RESULTS

A. Verification Setup

To ensure that the design works correctly, a testbench file was used to simulate an environment. The testbench just provides a 10 ns clock cycle as well as a reset signal at the start to reset the pipeline to known state. It logs the time, program counter, and reads the registers from the register module. It also logs which command is currently being used in the writeback stage to verify that the registers are updating correctly when a command runs. The actual instructions aren't located in the testbench file, but rather the instruction memory module. This is due to the fact that in realistic RISC architecture, processors always read the instructions from the instruction memory, so the testbench just needs to provide the simulation environment. The instruction memory module then loads the instructions into memory to verify all 10 operations as well as the forwarding and hazard units. This ensures that the system works as expected and remains stable. Comments were added in the instruction memory module to specify the exact MIPS instruction. Fig. 2 shows the simulated 32-bit Pipelined MIPS RTL Diagram, which confirms that the modules and multiplexers are connected correctly.

B. Functional Analysis

Fig. 3 shows the functional simulation log and Fig. 4 shows the corresponding instructions in memory. According to Fig. 3, when the Program Counter (PC) increments from 0 to 12, the pipeline is currently being reset due to the reset signal from the testbench and there is no operation (NOP). PC=16 is when the first operation is tested, which is the addi

command. Five and zero are added into the (\$t0) register, which updates correctly in the next PC cycle ($5 + 3 = 8$). PC=20 to PC=36 also successfully calculates logical operations like AND and OR and saves to the correct registers. At PC=52, a specific test was performed with a negative number ($0 + -5 = -5$) to ensure that the immediate handler can handle negative numbers in 2's complement, which it passed and saved the correct result (-5) into register (\$t3).

At PC=56, the branch instruction was tested. Looking at the instruction from memory, since registers (\$t2) and (\$t6) are both equal to 8, the next two instructions should be skipped. The branch was successful because (\$t0) and (\$t1) did not update to 99 and kept its original value.

At PC=68, the jump instruction was tested and was successful because it jumped to address 15 and skipped the next instruction since (\$t2) did not update to 99 and kept its original value. At the end of the test after PC=72, since there are no more instructions in memory, the jump command was used to create an infinite loop to prevent the program from crashing. At the end of the program, the PC loops between 68 and 72, which also verifies that the jump instruction works as expected.

C. Hazard and Forwarding Logic

Fig. 3 and Fig. 4 also demonstrate that the hazard and forwarding logic are working as expected. Looking at PC=40 and PC=44, the store word and load word instructions work as expected because the value of (\$t2) is first stored in memory address 0. The load word command then correctly loads 8 into the register (\$t6) from that same address. The next add instruction then uses register (\$t6) right after outputting the correct result ($8 + 3 = 11$), proving that the system remains stable during "load-use" conflicts. At PC=36, the clock stalls for one clock cycle. This proves that the hazard detection unit accurately detects the "load-use" conflict and stalls the system for one clock cycle. The reason why the stall shows at PC=36 and not PC=48 is because PC=36 is when the add instruction is fetched in the pipeline. The logging logic just prints the output at the writeback stage, which is 4 stages behind the instruction fetch stage.

At PC=68, an add instruction is run to calculate a result ($5 + 3 = 8$) and saved to register (\$t8). At PC=72, a subtraction instruction then uses that same register (\$t8) right after to calculate a new output to register (\$t9). Looking at register (\$t9), the output is correct ($8 - 5 = 3$), which proves that the forwarding module prevents the pipeline from using outdated values in the case of a data hazard.

CONCLUSION

In conclusion, the project successfully designed and verified a functional 32-bit pipelined MIPS processor using SystemVerilog. By following a modular approach, the system and code became more organized and easier to debug. The design choice to use a 5 stage pipeline made the processor more efficient since it can process multiple instructions at the same time. Processor reliability is extremely important since a mistake in the pipeline could confuse the rest of the system, so the hazard detection unit

and a forwarding unit proved that the system can handle complex data hazards and “load-use” conflicts reliably.

The simulation results confirm that all of the instructions work as intended, from the basic math and logic operations to branch and jump operations. Overall, this project demonstrates reliable data hazard handling and modular RISC architecture are effective for modern computer processing.

ACKNOWLEDGMENT

This project was completed with the guidance of Dr. Balasubramaniyan Chandrasekaran and Dr. Anshul Jha at the University of the Pacific.

REFERENCES

- [1] J. L. Hennessy and D. A. Patterson, Computer Architecture: A Quantitative Approach, 6th ed. Cambridge, MA: Morgan Kaufmann, 2017. A
- [2] T. J. Sparks, Pipelined MIPS Processor, GitHub repository